

Formulae in Circuit Theory

1. Chapter 1

$$i(t) = \frac{dq(t)}{dt},$$

i : the current in amperes (A),

q : the charges in coulombs (C),

t : the time in seconds (s).

$$v(t) = \frac{dw(t)}{dq}$$

v : the voltage in volts (V),

w : the energy in joules (J),

q : the charge in coulombs(C).

$$p(t) = \frac{dw(t)}{dt}$$

p : the power in watts (W),

w : the energy in joules (J),

t : the time in seconds (s).

$$p(t) = \frac{dw}{dt} = \left(\frac{dw}{dq}\right)\left(\frac{dq}{dt}\right) = v(t)i(t),$$


p : the power in watts (W),

v : the voltage in volts (V),

i : the current in amperes(A).


2. Chapter 2

Ohm's Law

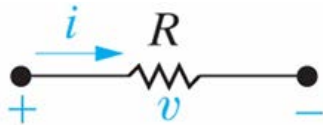

$$v = iR$$

$$p = vi = \frac{v^2}{R} = i^2 R$$

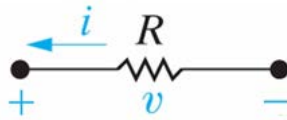

$$v = -iR$$

$$p = -vi = \frac{v^2}{R} = i^2 R$$

Kirchhoff's Current Law (KCL)

$$\sum_{\text{at any node}} i = 0$$

$$\text{or } \sum i_{\text{leaving}} - \sum i_{\text{entering}} = 0 \text{ at any nodes}$$

$$\text{or } \sum i_{\text{leaving}} = \sum i_{\text{entering}} \text{ at any nodes}$$

Kirchhoff's Voltage Law (KVL)

$$\sum_{\text{along any closed loop}} v = 0$$

$$\text{or } \sum v_{\text{drop}} - \sum v_{\text{rise}} = 0 \text{ along any closed loops}$$

$$\text{or } \sum v_{\text{drop}} = \sum v_{\text{rise}} \text{ along any closed loops}$$

3. Chapter 3

n resistors in series connection

$$R_{eq} = R_1 + R_2 + \cdots + R_{n-1} + R_n$$


n resistors in parallel connection

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_{n-1}} + \frac{1}{R_n}$$

Voltage divider circuits

$$v_1 = R_1 i = \frac{R_1}{R_1 + R_2} v_s$$

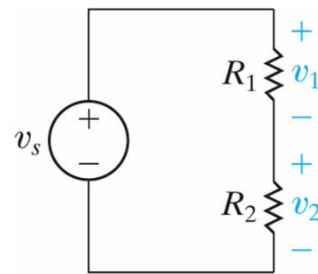
$$v_2 = R_2 i = \frac{R_2}{R_1 + R_2} v_s$$




Current divider circuits

$$i_1 = \frac{v}{R_1} = \frac{R_2}{R_1 + R_2} i_s$$
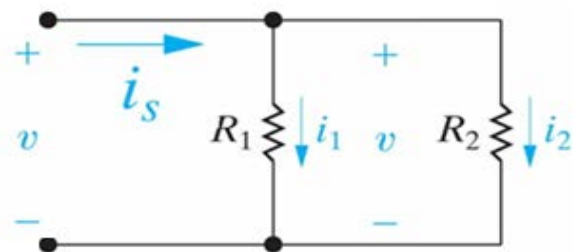
$$i_2 = \frac{v}{R_2} = \frac{R_1}{R_1 + R_2} i_s$$




4. Chapter 4

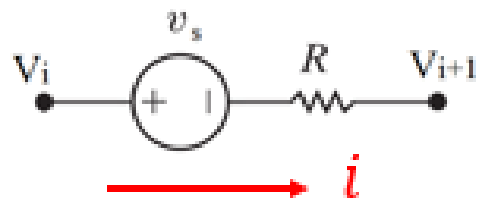

In general, the current in the above branch can be found as


$$i = \frac{V_i - v_s - V_{i+1}}{R}$$

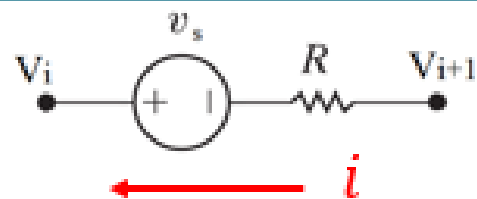

In general, the current in the above branch can be found as

$$i = \frac{V_{i+1} + v_s - V_i}{R}$$

The source transformation

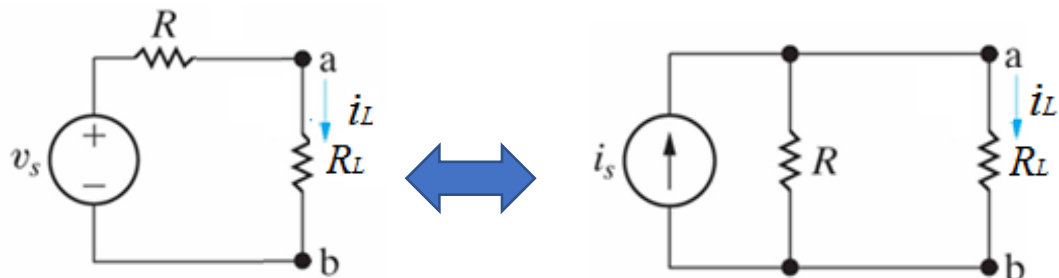

$$v_s = R i_s$$

$$R_v = R_i$$

5. Chapter 5

For an ideal op-amp

$$v_p = v_n, \quad i_p = i_n = 0 \quad CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

6. Chapter 6

Inductors	
$v = L \frac{di}{dt}$	(V)
$i = \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0)$	(A)
$p = vi = Li \frac{di}{dt}$	(W)
$w = \frac{1}{2} Li^2$	(J)
Series-Connected	
$L_{eq} = L_1 + L_2 + \cdots + L_n$	
Parallel-Connected	
$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_n}$	
$i(t_0) = i_1(t_0) + i_2(t_0) + \cdots + i_n(t_0)$	

Capacitors	
$v = \frac{1}{C} \int_{t_0}^t i \, d\tau + v(t_0)$	(V)
$i = C \frac{dv}{dt}$	(A)
$p = vi = Cv \frac{dv}{dt}$	(W)
$w = \frac{1}{2} C v^2$	(J)
Series-Connected	
$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n}$	
$v(t_0) = v_1(t_0) + v_2(t_0) + \cdots + v_n(t_0)$	
Parallel-Connected	
$C_{eq} = C_1 + C_2 + \cdots + C_n$	

7. Chapter 12

Table 1, 2 and 3. These tables will be given in quizzes and the final exam.

8. Chapter 13

If the source of the circuit is $x(t) = A \cos(\omega t + \phi)$, the steady-state response to the source is $y_{ss}(t)$, the transfer function is $H(s) = \frac{Y_{ss}(s)}{X(s)}$, then

$$y_{ss}(t) = A|H(j\omega)|\cos [\omega t + \phi + \theta(\omega)]$$

where $H(j\omega)$ is the transfer function, $H(s) = \frac{Y_{ss}(s)}{X(s)}$, of the circuit when $s = j\omega$. $H(j\omega) = |H(j\omega)|e^{j\theta(\omega)}$, where $|H(j\omega)|$ and $\theta(\omega) = \angle H(j\omega)$ is the magnitude and phase angle of $H(j\omega)$, respectively.