

Laboratory 2: Resistor Combinations, KCL, KVL, Voltage and Current Dividers

Adrian Darian, Elaine Huang, Federico Del Castillo Carnero

9/16/2020

Objectives

- Verify KCL and KVL
- Measure resistor combinations
- Measure branch currents and node voltages

Equipment and Components


- A computer
- Matlab software

Preliminary

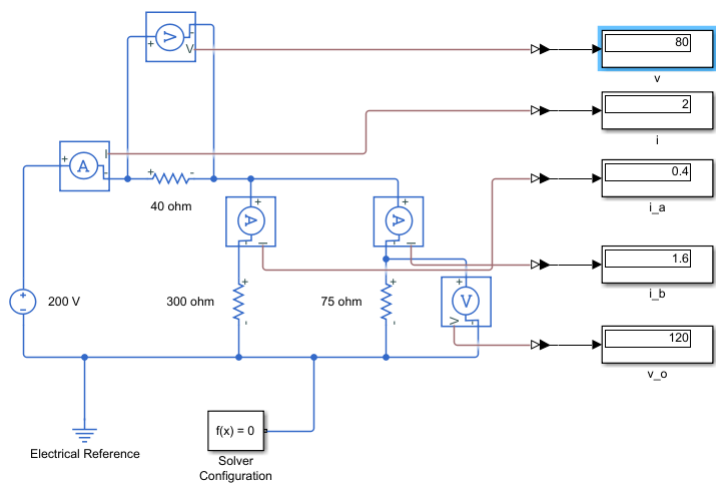1. Refer to Chapters 2 and 3 of the textbook if necessary.
2. Complete the theoretical calculations related to this lab.

Procedure


- 1 Open Matlab
- 2 Create Simulink model of the circuit shown below by following the procedure in Lab 1
- 3 Fill up your simulation results in the following table.



| Source = 200V | Simulation Results | Theoretical Results |
|---------------|--------------------|---------------------|
| i | 2A | 2A |
| i_a | 0.4A | 0.4A |
| i_b | 1.6A | 1.6A |
| v | 80V | 80V |
| v_o | 120V | 120V |

$$\begin{aligned}
 i_a &= \frac{v_o}{R_g} \\
 &= \frac{120}{300} \\
 &= 0.4A \\
 i_b &= \frac{v_o}{R_b} \\
 &= \frac{120}{75} \\
 &= 1.6A \\
 i &= i_a + i_b \\
 &= 2A \\
 v_o &= \frac{v_o - v_g}{R_g} + \frac{v_o}{R_a} + \frac{v_o}{R_b} \\
 &= 120V \\
 v &= v_s - v_o \\
 &= 80V
 \end{aligned}$$

- What is the sum of i_a and i_b ? Sum = 2. What is i ? Explain.
Answer: i is the initial current flowing out of the voltage source. Also Current does not change when passing through resistors it only splits at forks in the circuit.
- What is the sum of v and v_o ? Sum = 200. Explain.
- Are your simulation results consistent with your theoretical results of Problem 2.18 in Assignment 2?
- Set the voltage source to be 100V and repeat the above steps. Fill up the table below. Comparing the results in Table 2 with those in Table 1, what do you find?
Answer: We found that when comparing the results between a 200V and a 100V source the 100V is exactly half the readings of the 200V

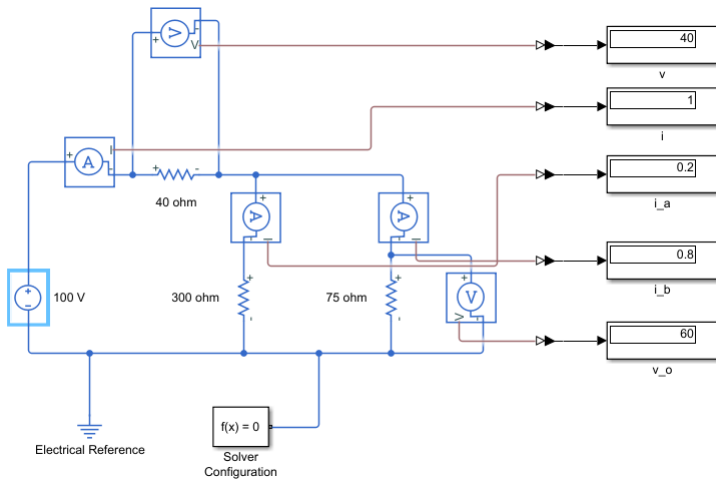


| Source = 100V | Simulation Results | Theoretical Results |
|---------------|--------------------|---------------------|
| i | 1A | 1A |
| i_a | 0.2A | 0.2A |
| i_b | 0.8A | 0.8A |
| v | 40V | 40V |
| v_o | 60V | 60V |

$$\begin{aligned}
 i_a &= \frac{v_o}{R_g} \\
 &= \frac{120}{300} \\
 &= 0.2A \\
 i_b &= \frac{v_o}{R_b} \\
 &= \frac{120}{75} \\
 &= 0.8A \\
 i &= i_a + i_b \\
 &= 1A \\
 v_o &= \frac{v_o - v_g}{R_g} + \frac{v_o}{R_a} + \frac{v_o}{R_b} \\
 &= 60 \\
 v &= v_s - v_o \\
 &= 40
 \end{aligned}$$

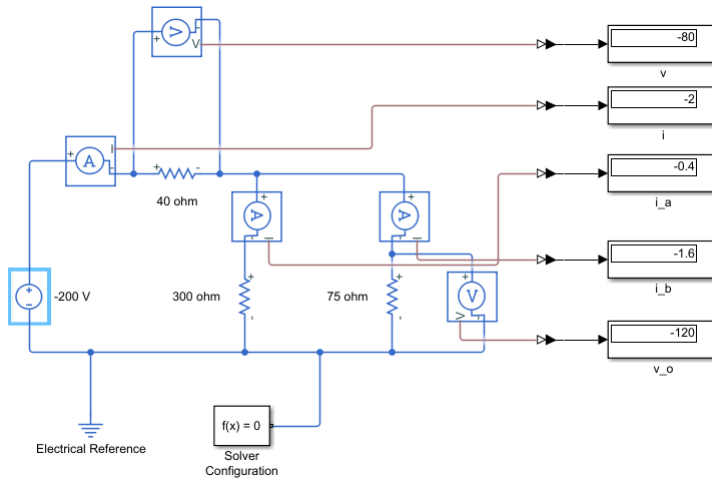e. Set the voltage source to be $-200V$ repeat the above steps 1, 2, and 3. Fill up the table below. Comparing the results in Table 3 with those in Table 1, what do you find?


Answer: We found that when comparing the results between a 200V and a $-200V$ source the $-200V$ contains the same results except negative of the 200V



| Source = $-200V$ | Simulation Results | Theoretical Results |
|------------------|--------------------|---------------------|
| i | $-2A$ | $-2A$ |
| i_a | $-0.4A$ | $-0.4A$ |
| i_b | $-1.6A$ | $-1.6A$ |
| v | $-120V$ | $-120V$ |
| v_o | $-120V$ | $-120V$ |

$$\begin{aligned}
 i_a &= \frac{v_o}{R_g} \\
 &= \frac{120}{300} \\
 &= -0.4A \\
 i_b &= \frac{v_o}{R_b} \\
 &= \frac{120}{75} \\
 &= -1.6A \\
 i &= i_a + i_b \\
 &= -2A \\
 v_o &= \frac{v_o - v_g}{R_g} + \frac{v_o}{R_a} + \frac{v_o}{R_b} \\
 &= -120V \\
 v &= v_g - v_o \\
 &= -80V
 \end{aligned}$$

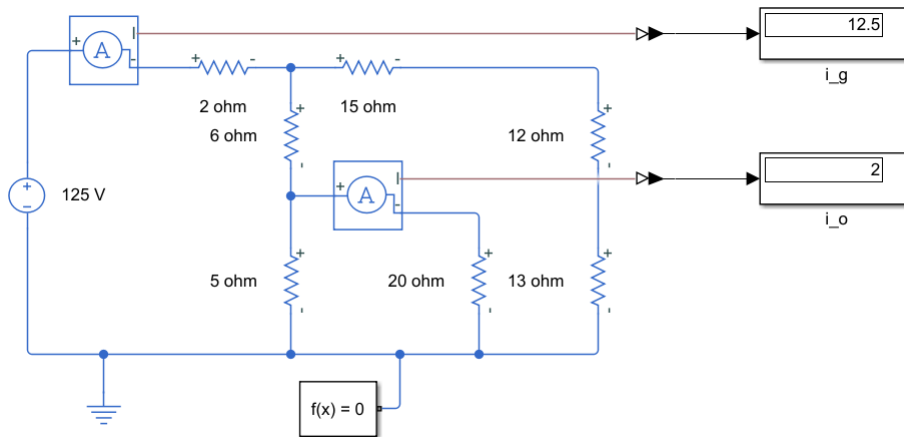
4 Create the Simulink of the following circuit and find i_g and i_o . Fill up the table shown below. Are the simulation solutions with your theoretical solutions of Problem 3.28 in Assignment 3?



| | Simulation Results | Theoretical Results |
|-------|--------------------|---------------------|
| i_g | 12.5A | 12.5A |
| i_o | 2A | 2A |

$$\begin{aligned}
 i_i &= \frac{i_g * (12+13+15)}{10+(12+13+15)} \\
 &= 10A \\
 i_o &= \frac{i_i * 5}{20+5} \\
 &= 2A \\
 i_g &= \frac{125}{2+8} \\
 &= 12.5A
 \end{aligned}$$

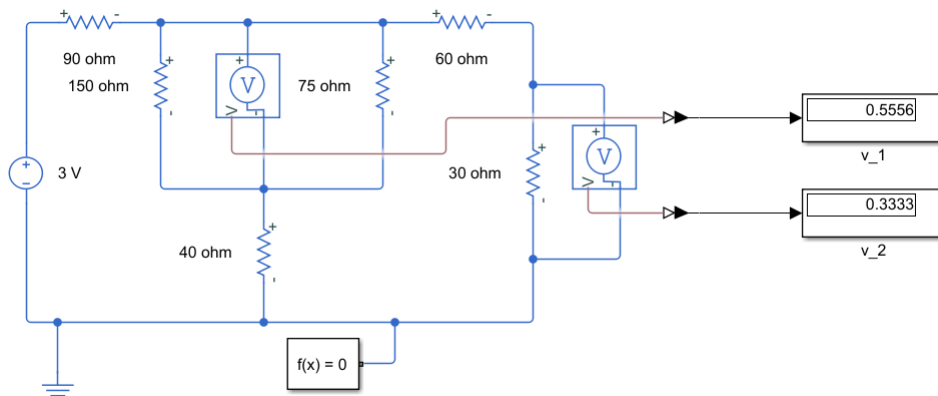- 5 Create the Simulink model of the following circuit and find v_1 and v_2 . Are the simulation solutions consistent with your theoretical solutions of Problem 3.30 in Assignment 3? Fill up the table shown below.



| | Simulation Results | Theoretical Results |
|-------|--------------------|---------------------|
| v_1 | 0.5556V | 0.5556V |
| v_2 | 0.3333V | 0.3333V |

$$\begin{aligned}
 v_1 &= (150||75)||((150||75) + 40) \\
 &= 0.5556V \\
 v_2 &= \frac{30}{30+60} \\
 &= 0.3333V
 \end{aligned}$$

Questions and Conclusions

- Use tables and graphs to explain your results.
- Summarize your findings and explanations in response to the questions posed in this lab.
Answer: The first few circuit diagrams we created in lab allowed us to observe the change in voltage and current across the whole system, through changing the voltage source potential. In the 2nd circuit we got to observe the change in current and found that the current drastically decreased as the voltage passed through the circuit. In the 3rd circuit we got to observe the change in voltage as we added more resistors in series and in parallel to the circuit diagram.