


Assignment 2

Adrian Darian

9/11/2020

Chapter 2

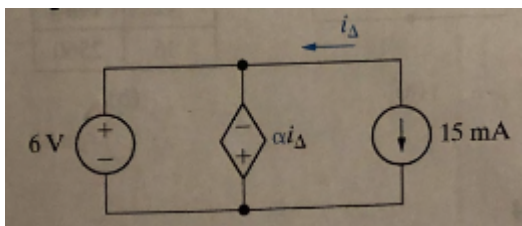6 Consider the interconnection shown in the figure below.



a) What value of α is required to make this a valid interconnection?


$$\begin{aligned} \alpha &= \frac{-6\text{ V}}{-15\text{ mA}} \\ &= 400 \end{aligned}$$

b) For this value of α , find the power associated with the current source.

$$\begin{aligned} p &= V * i \\ &= 6\text{ V} * 15\text{ mA} \\ &= 90\text{ mW} \end{aligned}$$

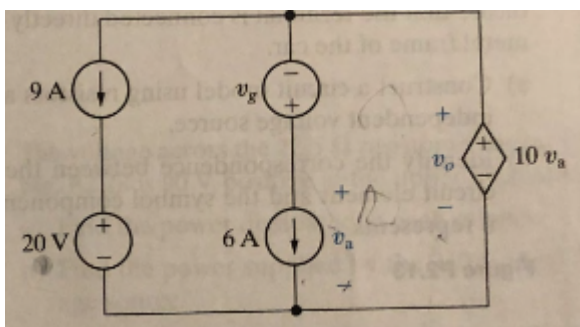
c) Is the current source supplying or absorbing power?
absorbing

9 Find the total power developed in the circuit in the figure below if $v_o = 5\text{ V}$



$$\begin{aligned}
10v_a &= v_o \\
v_a &= 0.5 \text{ V} \\
i_{v_a} &= 15 \text{ A} \\
v_g &= v_a - v_o \\
&= 0.5 \text{ V} - 5 \text{ V} \\
&= -4.5 \text{ V} \\
P_{v_g} &= v_g * 6 \\
&= (-4.5) * 6 \\
&= -27 \text{ W} \\
v_{9A} &= -15 \text{ V} \\
P_{9A} &= -15 * 5 \\
&= -75 \text{ W} \\
P_{20V} &= 20 * 9 \\
&= 180 \text{ W} \\
P_{v_o} &= -(9 \text{ V}) * (15 \text{ A}) \\
&= -135 \text{ W} \\
P_{total} &= 210 \text{ W}
\end{aligned}$$

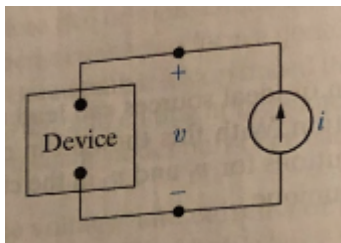15 A variety of current source values were applied to the device shown in the figure below




i mA	p mW
0.5	8.25
1.0	33.00
1.5	74.25
2.0	132.00
2.5	206.25
3.0	297.00


a) The power absorbed by the device for each value of current is recorded in the table given in the table above.

i mA	p mW	$R = \frac{p}{i^2}$ k Ω
0.5	8.25	33
1.0	33.00	33
1.5	74.25	33
2.0	132.00	33
2.5	206.25	33
3.0	297.00	33

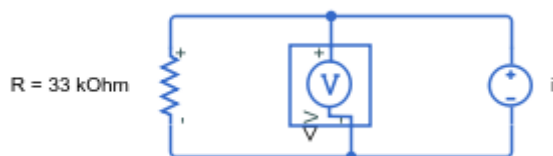b) Use the values in the table to construct a circuit model for the device consisting of a single resistor.



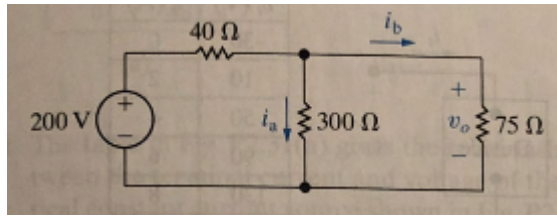18 Given the circuit shown in the figure below, find



a) the value of i_a

$$\begin{aligned} i_a &= \frac{v_o}{R_a} \\ &= 0.4 \text{ A} \end{aligned}$$

b) the value of i_b

$$\begin{aligned} i_b &= \frac{v_o}{R_b} \\ &= 1.6 \text{ A} \end{aligned}$$

c) the value of v_o

$$\begin{aligned} \frac{v_o - v_g}{R_g} + \frac{v_o}{R_a} + \frac{v_o}{R_b} &= 0 \\ \frac{v_o - 200}{40} + \frac{v_o}{300} + \frac{v_o}{75} &= 0 \\ v_o &= 120 \text{ V} \end{aligned}$$


d) the power dissipated in each resistor

$$\begin{aligned} P_g &= \left(\frac{v_g - v_o}{R_g} \right)^2 * R_g \\ &= 160 \text{ W} \\ P_{R_a} &= i_a^2 * R_a \\ &= 48 \text{ W} \\ P_{R_b} &= i_b^2 * R_b \\ &= 192 \text{ W} \end{aligned}$$

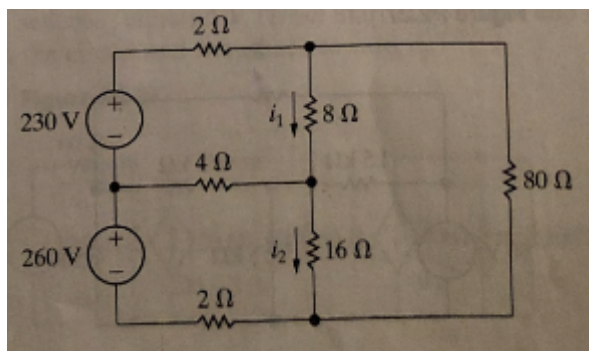e) the power delivered by the 200 V source

$$\begin{aligned} P_g &= V_g * I_g \\ &= 200 * \frac{200 - 120}{40} \\ &= 400 \text{ W} \end{aligned}$$

24 The currents i_1 and i_2 in the circuit in the figure below are 20 A and 15 A, respectively




a) Find the power supplied by each voltage source.

$$\begin{aligned}
-230 + 2i_1 + 8(i_1 - i_3) + 4(i_1 - i_2) &= 0 \\
-260 + 2i_2 + 4(i_2 - i_1) + 16(i_2 - i_3) &= 0 \\
8(i_3 - i_1) + 16(i_3 - i_2) + 80i_3 &= 0 \\
i_1 &= 25 \text{ A} \\
i_2 &= 20 \text{ A} \\
i_3 &= 5 \text{ A} \\
P_{230} &= 230i_1 \\
&= 5750 \text{ W} \\
P_{260} &= 260i_2 \\
&= 5200 \text{ W}
\end{aligned}$$

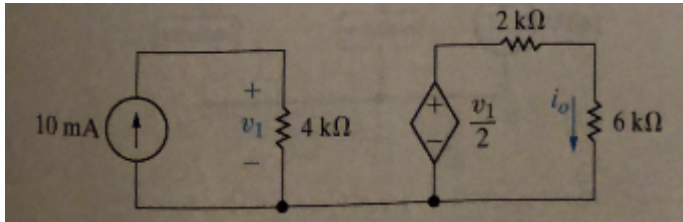b) Show that the total power supplied equals the total power dissipated in the resistors.

$$\begin{aligned}
P_T &= P_{230} + P_{260} \\
&= 10.950 \text{ W} \\
P_d &= 2i_a + 8i_1 + 4(i_a - i_b) + 2i_b + 16i_2 + 80i_c \\
&= 1250 + 3200 + 100 + 800 + 3600 + 2000 \\
&= 10.590 \text{ W}
\end{aligned}$$

32 Consider the circuit shown in the figure below.



a) Find i_o

$$\begin{aligned}
V_1 &= 10 \text{ mA} * 4 \text{ k}\Omega \\
&= 40 \text{ V} \\
i_o &= \frac{\frac{V_1}{2}}{2 \text{ k}\Omega + 6 \text{ k}\Omega} \\
&= 2.5 \text{ mA}
\end{aligned}$$

b) Verify the value of i_o by showing that the power generated in the circuit equals the power absorbed in the circuit.

$$\begin{aligned}
P_{generated} &= \frac{V_1}{2} * 2.5 \text{ mA} \\
&= 50 \text{ mW} \\
P_{absorbed} &= (2 \text{ k}\Omega + 6 \text{ k}\Omega) * i_o^2 \\
&= 50 \text{ mW}
\end{aligned}$$