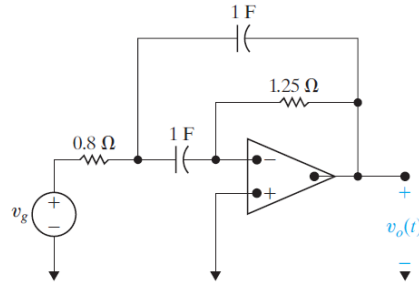



## Example #5 (p13.48)



Find  $v_o(t)$  in the circuit shown above if the ideal op amp operates within its linear range and  $v_g = 4.8u(t)$  mV. (The initial energy stored in the circuit is zero)
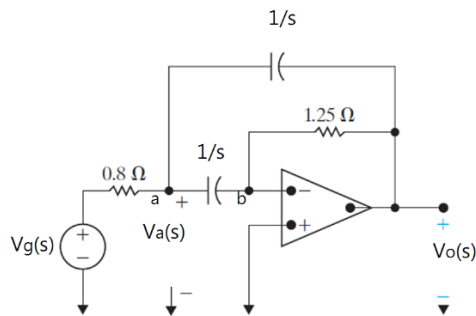
### Solution:

Because the initial energy stored in the circuit is zero, the voltages across the two capacitors in the above circuit, at  $t = 0^+$ , are equal to zero. Therefore, the circuit in the s domain is



Because the op amp is ideal,  $I_n = I_p = 0$  and  $V_n = V_p$ . Here  $V_p = 0$ , so  $V_n = 0$ .

Writing the node-voltage equations at node **a** and **b**, we have:

$$\frac{V_a(s) - V_g(s)}{0.8} + \frac{V_a(s) - V_o(s)}{1/s} + \frac{V_a(s) - V_n(s)}{1/s} = 0 \quad (1)$$

$$\frac{V_n(s) - V_a(s)}{1/s} + \frac{V_n(s) - V_o(s)}{1.25} = 0 \quad (2)$$

From (2), we have:

$$V_a(s) = -\frac{V_o(s)}{1.25s} \quad (3)$$

From (1), we have:

$$V_a(s) \left( \frac{1}{0.8} + s + s \right) - sV_o(s) = \frac{V_g(s)}{0.8} \quad (4)$$

Plugging (3) into (4), yield:

$$-\frac{V_o(s)}{1.25s} \left( \frac{1}{0.8} + 2s \right) - sV_o(s) = \frac{V_g(s)}{0.8} \quad (5)$$

From (5), we have:

$$V_o(s) \left( \frac{s^2 + 1.6s + 1}{s} \right) = -1.25V_g(s) \quad (6)$$

Plugging  $V_g(s) = \mathcal{L}\{v_g\} = \frac{4.8}{s}$  into (6), yield:

$$V_o(s) \left( \frac{s^2 + 1.6s + 1}{s} \right) = -1.25 \times \frac{4.8}{s}$$

Therefore:

$$\begin{aligned} V_o(s) &= \frac{-6}{s^2 + 1.6s + 1} = \frac{-6}{(s^2 + 1.6s + 0.64) + 0.32} = \frac{-6}{(s + 0.8 - j0.6)(s + 0.8 + j0.6)} \\ &= \frac{k}{s + 0.8 - j0.6} + \frac{k^*}{s + 0.8 + j0.6} \\ k &= V_o(s)(s + 0.8 - j0.6)|_{s=-0.8+j0.6} = j5 = 5e^{j90^\circ} \end{aligned}$$

The output voltage of the circuit is

$$v_o(t) = 2 \times 5e^{-0.8t} \cos(0.6t + 90^\circ) = 10e^{-0.8t} \cos(0.6t + 90^\circ) u(t) \text{ V}$$