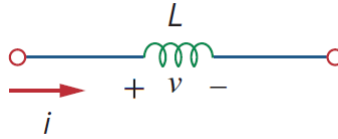


Assignment 8


1. The voltage across a 50 mH inductor is given by




$$v(t) = (5e^{-2t} + 2t + 4) \text{ V for } t > 0.$$

Determine the current $i(t)$ through the inductor. Assume that $i(0) = 0 \text{ A}$.

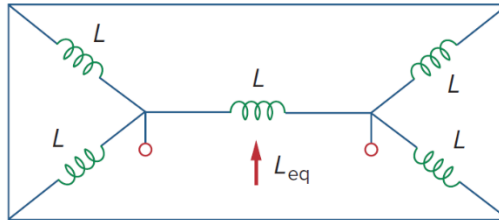
2. Find L_{eq} in each of the following circuit.



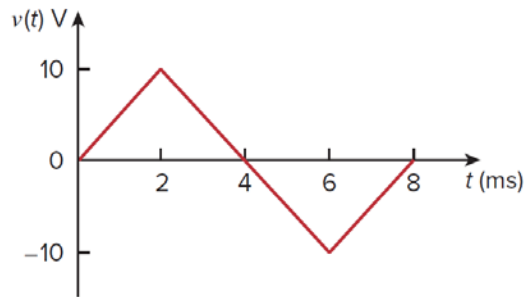
3. The voltage across a $4 \mu\text{F}$ capacitor is shown in the following figure. Find the current waveform. (Assume the current passing through the capacitor is along the voltage drop on it.)



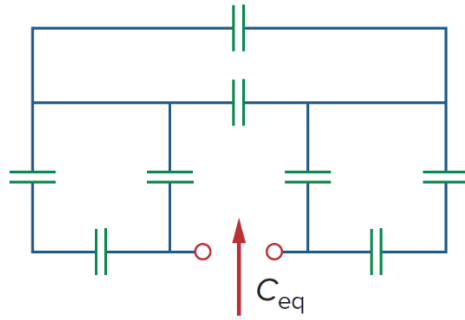4. Find C_{eq} in the circuit shown below if all capacitors are $4 \mu\text{F}$. (Note: around the solution to 2 decimal places)




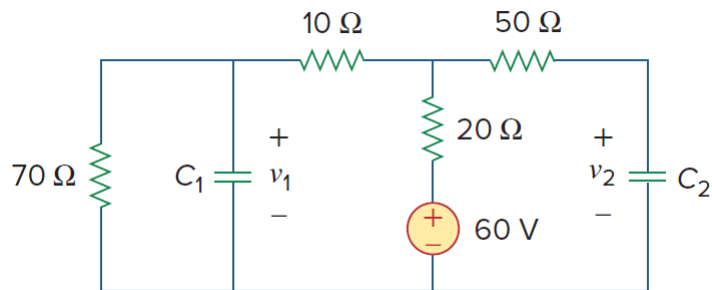5. Find the voltages across the capacitors in the circuit below under dc conditions. (Hints: When capacitors are fully charged, the voltages across the capacitors are constant)



Answers: $v_1 = 42\text{ V}$, $v_2 = 48\text{ V}$

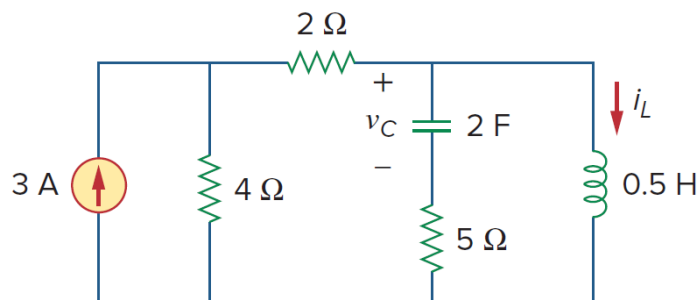6. Find v_C , i_L , and energy stored in the capacitor and inductor in the following circuit under dc conditions. (Hint: 1. When capacitors are fully charged, the voltages across the capacitors are constant. 2. When inductors have been driven by dc sources for a long time, the currents in the inductors are constant).



Answers: $v_C = 0$, $i_L = 2\text{ A}$, $w_C = 0\text{ J}$, $w_L = 1\text{ J}$