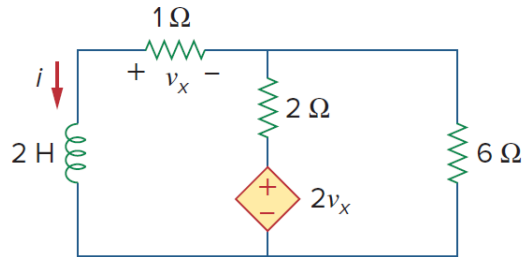



# Solutions of Assignment 12

1. Find  $i(t)$  and  $v_x(t)$  in the circuit below. Assume  $I_0 = i(0^-) = 12 \text{ A}$ .




**Answer:**  $i(t) = 12e^{-2t} \text{ A}$ ,  $v_x(t) = -12e^{-2t} \text{ V}$  for  $t > 0$ .

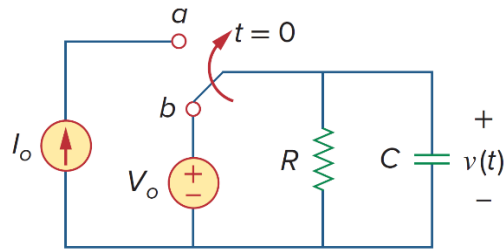2. The switch in the following circuit has been in position **b** for a long time. It is moved to position **a** at  $t = 0$ . Determine  $v(t)$  for  $t > 0$ .



**Answer:**  $v(t) = (V_0 - I_0 R)e^{-\frac{t}{\tau}} + I_0 R$ ,  $t > 0$ , where  $\tau = RC$ .

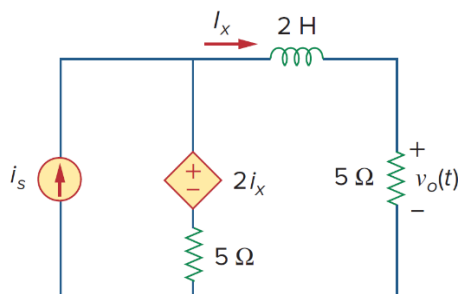3. Assume there is no initial energy stored in the circuit below at  $t = 0$  and that  $i_s = 10 \text{ u}(t) \text{ A}$ .



- a. Use Thevenin's theorem to find  $V_o(s)$ .

(Hints: Remove  $5 \Omega$  resistor and find  $V_{Th} = V_{oc}$ . Short  $5 \Omega$  resistor to find  $I_{sc}$  by using the node-voltage method, then  $Z_{Th} = \frac{V_{Th}}{I_{sc}}$ .)

- b. Find the transfer function of  $H(s) = \frac{V_o(s)}{I_s(s)}$


- c. Applying the initial- and final- value theorems to find  $v_o(0^+)$  and  $v_o(\infty)$ .

- d. Determine  $v_o(t)$ .  
 e. If  $i_s = 20 \cos(4t + 30^\circ) u(t)$  A, determine the steady-state response  $v_{oss}(t)$ .

**Answer:**  $v_o(t) = 31.25(1 - e^{-4t})u(t)$  V;  $v_{oss}(t) = 31.25\sqrt{2} \cos(4t - 15^\circ)$  V

4. In the op-amp circuit below,  $v_s(t) = 10u(t)$ . Assume that  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C_1 = 20 \text{ }\mu\text{F}$ , and  $C_2 = 100 \text{ }\mu\text{F}$ . The op-amp in the circuit is ideal. The initial anergy stored in the circuit is zero.

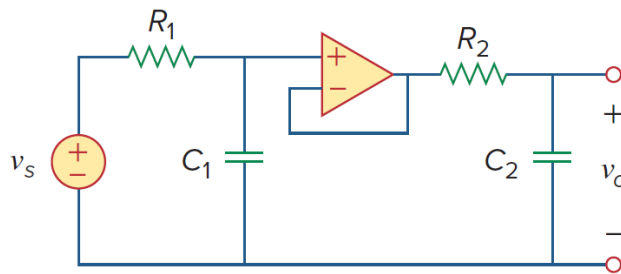- a. Find the transfer function  $H(s) = \frac{V_o(s)}{V_s(s)}$ .  
 b. Determine the type of the circuit response based on the transfer function.  
 c. Determine  $v_o(t)$  for  $t > 0$ .



**Answer:**  $v_o(t) = (10 - 12.5e^{-t} + 2.5e^{-5t})u(t)$  V