

## Laboratory 9

# Transient Responses of Second Order RLC Circuits

## Objectives

- Observe the transient responses of RLC circuits.
- Learn how R, L, and C affect the circuit behaviors.

## Equipment and components

- A desk computer
- PSPICE software


## Preliminary

- Read the lecture slides of “Inverse Laplace Transform and RC, RL, and RLC Circuits”.
- Find the voltage across a capacitor in each circuit. Find Neper frequency  $\alpha$ , and resonant (radian) frequency  $\omega_0$  and damping factor  $\frac{\alpha}{\omega_0}$  for each circuit.
- Find the resistance of the resistor with which each circuit response (the voltage) is overdamped, underdamped, and critically damped.


## Procedure

### The Series RLC circuit

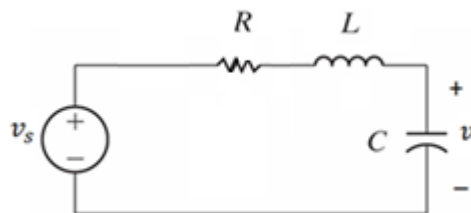1. Open PSpice and build the circuit shown below. Set  $L = 10\text{ mH}$ ,  $C = 0.01\text{ }\mu\text{F}$ , and  $R = 10\text{ k}\Omega$ .  $v_s$  is a pulse voltage source.



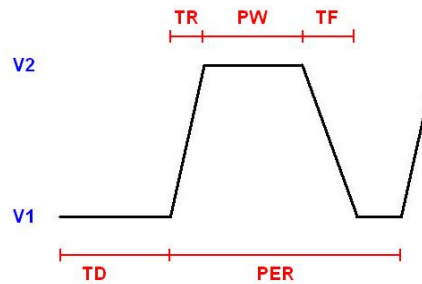2. Select VPULSE from Part box. The definitions of each parameters in VPULSE are shown below. Set  $V_1 = 0, V_2 = 10, TR = TF = TD = 0, PW = 1\text{ ms},$  and  $PER = 2\text{ ms}.$




3. If  $R = 10\text{ k}\Omega$ . What type of response do you obtain for the voltage?
4. Calculate  $R$  to obtain a critical response. What is the value of  $R$  when the circuit has the critically damped response.
5. Set  $R$  to  $500\text{ }\Omega$ . What type of response do you obtain for the voltage?
6. Measure the four major specifications that define the response of a second order system/circuit.

- 1) **The rise time ( $T_r$ )** is used to measure the swiftness of the circuit, which is defined as the time required reaching 90% of the reference input (the source).
- 2) **The overshoot (PO)** is used to measure the closeness of the response to the reference in terms of %. It is calculated as:

$$PO = ((M_p - \text{final value}) / \text{final value}) * 100$$

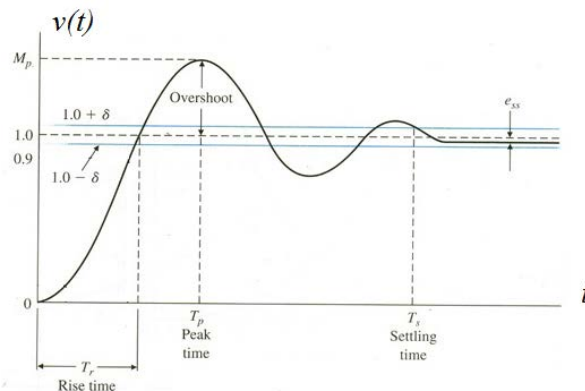
- 3) **The peak time ( $T_p$ )** measures the time taken to reach the maximum response.
- 4) **The settling time ( $T_s$ )** is the time required for the circuit to settle within a certain percentage of the reference input ( $\pm\delta$ ). Here, we choose  $\delta = 5\%$ .



**Note:** for critically and overdamped responses, only the rise time ( $T_r$ ) is required to measure.

## The parallel RLC circuit

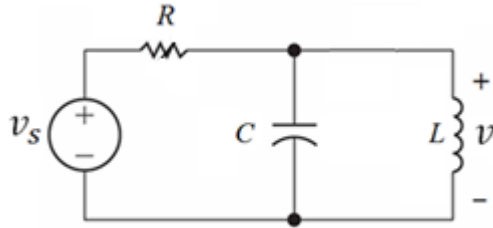1. Construct the circuit shown below in PSPICE.



2. Set  $L = 10 \text{ mH}$ ,  $C = 0.01 \text{ } \mu\text{F}$ , and  $R = 10 \text{ k}\Omega$ .
3. Set the source to be a square pulse and use the same parameters as described for the series RLC circuit.
4. If  $R = 10 \text{ k}\Omega$ . What type of response do you obtain for the voltage?
5. Find the value of  $R$  to result in a critically damped response.
6. Set  $R$  to be  $200 \text{ } \Omega$ . Observe the voltage response.
7. Compare the responses of the two circuits, explain why they are different for three different responses.

## Questions and conclusions

- Summarize your findings and explanations in response to the questions given in this lab.