





# Assignment 3

Adrian Darian

9/18/2020

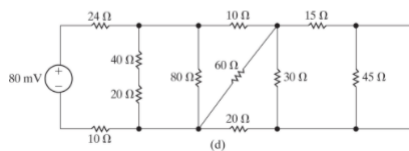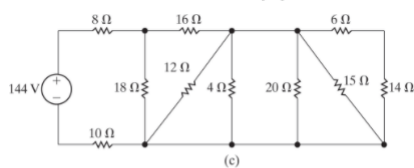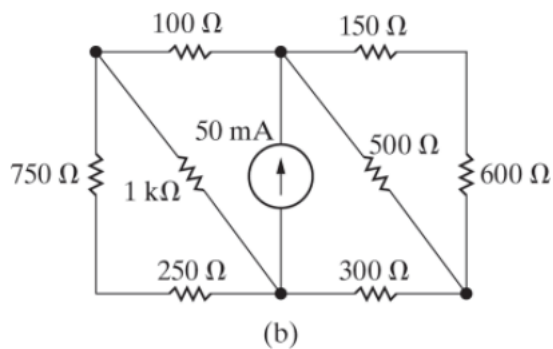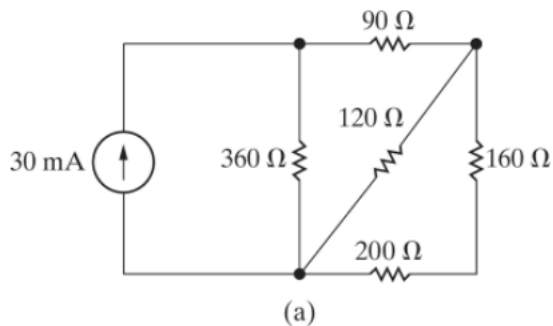
## Chapter 3

7 In the circuits in Fig. P3.7 (a)-(d), find the equivalent resistance seen by the source and the power delivered by the source.




- a) Resistance =  $360 || ((200 + 160) || 120 + (200 + 160) || 120) = 120 \Omega$   
 Power Delivered =  $120(30)^2 = 108mW$
- b) Resistance =  $((250 + 750) || 1000) + 100 || ((600 + 150) || 500 + (600 + 150) || 500) = 300 \Omega$   
 Power Delivered =  $300(50)^2 = 750mW$

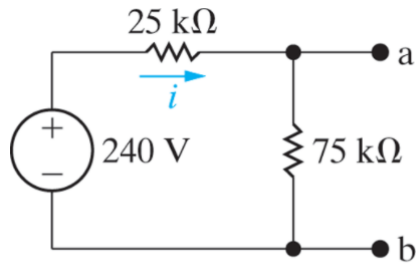- c) Resistance =  $8 + (18 \parallel (16 + (((6 + 14) \parallel 15) \parallel 20 \parallel 4) \parallel 12))) + 10 = 27 \Omega$   
 Power Delivered =  $\frac{(144)^2}{27} = 768W$
- d) Resistance =  $24 + (30 \parallel 60 \parallel 80) + (((15 \parallel 30) + 20) \parallel 60) = 6 \Omega$   
 Power Delivered =  $\frac{(144)^2}{27} = 106.67uW$
- 10 a) Find an expression for the equivalent resistance of two resistors of value  $R$  in series.  
 $R_{eq} = R + R = 2R$
- b) Find an expression for the equivalent resistance of  $n$  resistors of value  $R$  in series.  
 $R_{eq} = R + R + R + \dots + R = nR$
- c) Using the results of (a), design a resistive network with an equivalent resistance of  $3 \text{ k}\Omega$  using two resistors with the same value from Appendix H.  
 $R + R = 2R = 3000$   
 $R = 1500 \Omega$
- d) Using the results of (b), design a resistive network with an equivalent resistance of  $4 \text{ k}\Omega$  using a minimum number of identical resistors from Appendix H.  
 $nR = 4R = 4000$   
 $R = 1000 \Omega$
- 16 a) The voltage divider in Fig. P3.16 (a) is loaded with the voltage divider shown in Fig. P3.16 (b); that is,  $a$  is connected to  $a'$ , and  $b$  is connected to  $b'$ . Find  $v_o$ .



(a)

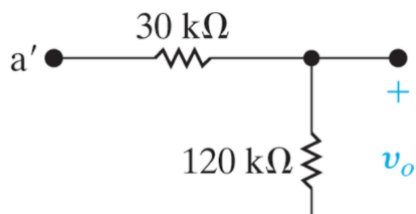


(b)

$$75k\Omega \parallel (120k\Omega + 30k\Omega) = 50k\Omega$$

$$v_{o1} = \frac{50k\Omega}{(75k\Omega)} * 240V = 160V$$

$$v_o = \frac{120k\Omega}{150k\Omega} * v_{o1} = 128V$$

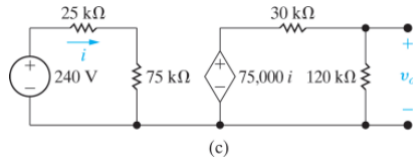- b) Now assume the voltage divider in Fig. P3.16 (b) is connected to the voltage divider in Fig. P3.16 (a) by means of a current-controlled voltage source as shown in Fig. P3.16 (c). Find  $v_o$ .




$$i = \frac{240V}{100k\Omega} = 2.4mA$$

$$v_o = \frac{120}{150} * 75000i = 144V$$

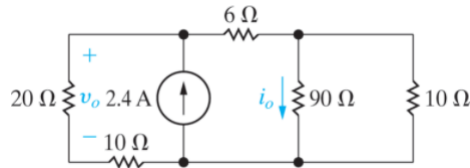- c) What effect does adding the dependent-voltage source have on the operation of the voltage divider that is connected to the 240 V source?

$$v_{o1} = 0.95 * 240V = 180V$$

19 For the current divider circuit in Fig. P3.19 calculate



- a)  $i_o$  and  $v_o$ .

$$\begin{aligned} R_{eq} &= (10 + 20) || (6 + (90 || 10)) \\ &= 10\Omega \\ v_{2.4A} &= 10i \\ &= 2.4 * 10 \\ &= 24V \\ v_o &= v_{20\Omega} \\ &= (24) * \frac{10}{10+20} \\ &= 16V \\ v_{90\Omega} &= 24 * \left( \frac{90 || 10}{6 + (90 || 10)} \right) \\ &= 14.4V \\ i_o &= \frac{v_{90\Omega}}{90} \\ &= 0.16A \end{aligned}$$


- b) the power dissipated in the 6 Ohm resistor.

$$P_{6\Omega} = \frac{(v_{2.4A} - v_{90\Omega})^2}{6} = \frac{(24 - 14.4)^2}{6} = 15.36W$$

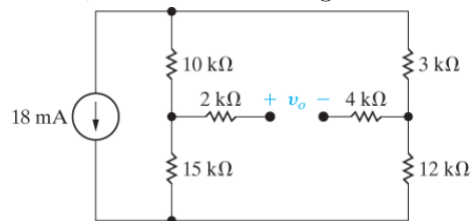
- c) the power developed by the current source.

$$P_{2.4A} = -(V_{2.4A})(i_{2.4A}) = -(24)(2.4) = -57.6W$$

31 Find  $v_o$  in the circuit in Fig. P3.31 using voltage and/or current division.


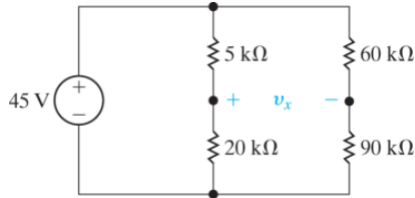
$$\begin{aligned}
i_1 &= \frac{-(18mA)(3k+12k)}{(3k+12k)+(10k+15k)} \\
&= -6.75mA \\
v_{15k} &= i_1(15k) \\
&= -101.25V \\
i_2 &= i_s - i_1 \\
&= -11.25mA \\
v_{12k} &= (i_{12k})(12k) \\
&= -135V \\
v_o &= v_{15k} - v_{12k} \\
&= 33.75V
\end{aligned}$$



32

- a) Find the voltage  $v_x$  in the circuit in Fig. P3.32 using voltage and/or current division.

$$\begin{aligned}
v_{20k} &= 45 * \frac{20k\Omega}{(20k\Omega+5k\Omega)} \\
&= 36V \\
v_{90k} &= 45 * \frac{90k\Omega}{(90k\Omega+60k\Omega)} \\
&= 27V \\
v_x &= v_{20k} - v_{90k} \\
&= 9V
\end{aligned}$$

- b) Replace the 45V source with a general voltage source equal to  $V_s$ . Assume  $V_s$  is positive at the upper terminal. Find  $v_x$  as a function of  $V_s$ .

$$\begin{aligned}
v_{20k} &= \frac{20k}{(20k+5k)}(V_s) \\
&= 0.8V_s \\
v_{90k} &= \frac{90k}{(90k+60k)}(V_s) \\
&= 0.6V_s \\
v_x &= v_{20k} - v_{90k} \\
&= 0.2V_s
\end{aligned}$$