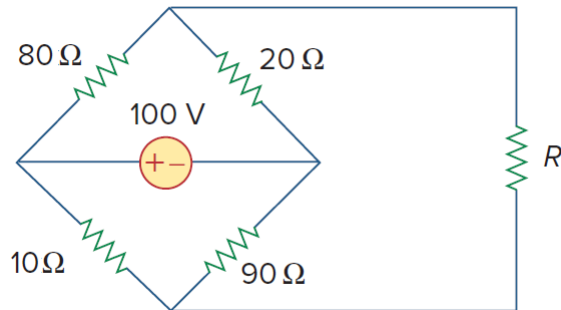



Assignment 6

1. The variable resistor R shown in the following figure is adjusted until it absorbs the maximum power from the circuit. (a) Calculate the value of R for the maximum power (b) Determine the maximum power absorbed by R .




Answer: (a) $R = 25\Omega$. (b) 49 W

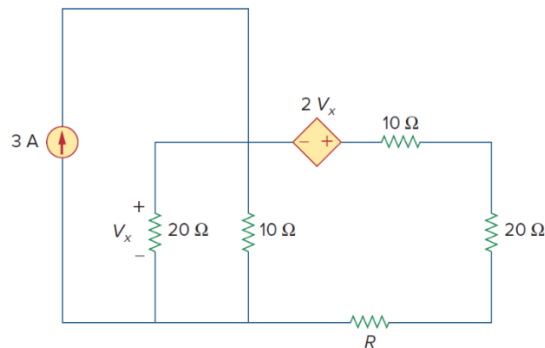2. Determine the maximum power delivered to the variable resistors R shown in the circuit shown below.




Answer: 18 W

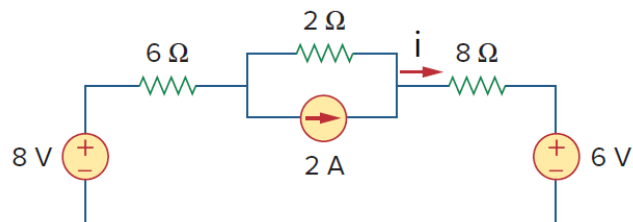3. Use the principle of superposition to find the current i in the following circuit and the power associated with the current source.



Answer: 375 mA.

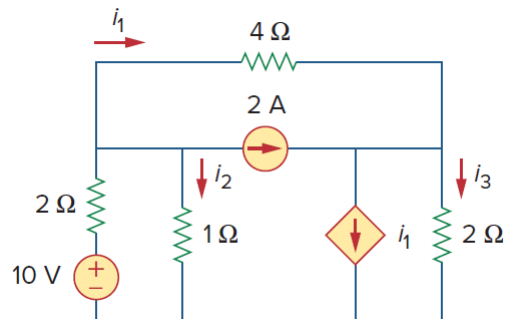4. Use the principle of superposition to find i_1 , i_2 , and i_3 .



Answer: $i_1 = -428.6 \text{ mA}$, $i_2 = 2.286 \text{ A}$, $i_3 = 2 \text{ A}$.