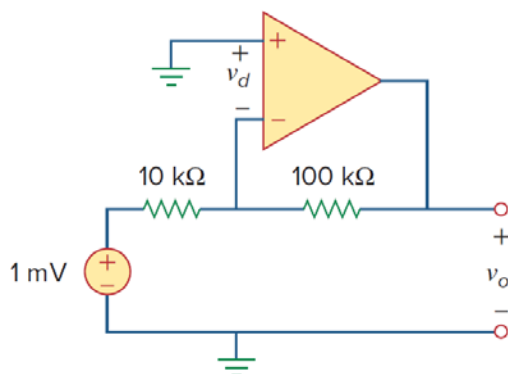


# Assignment 7

1. The inverting amplifier circuit is shown below.


- (a) If the input resistance of the op amp  $R_i = 100 \text{ k}\Omega$ , the output resistance of the op amp  $R_o = 100 \Omega$ , and the open loop gain of the op amp  $A = 100,000$ , find the differential voltage  $v_d = v_p - v_n$  and the output voltage  $v_o$ .
- (b) If the input resistance of the op amp  $R_i = \infty$ , the output resistance of the op amp  $R_o = 0 \Omega$ , and the open loop gain of the op amp  $A = \infty$ , find the differential voltage  $v_d = v_p - v_n$  and the output voltage  $v_o$ .
- (c) From the solutions from the above a and b, what can you conclude?

(Round the solutions to 2 decimal places)




**Answers: (a)  $v_d \approx -100 \text{ nV}$ ,  $v_o \approx -10 \text{ mV}$ . (b)  $v_o = -10 \text{ mV}$ .**

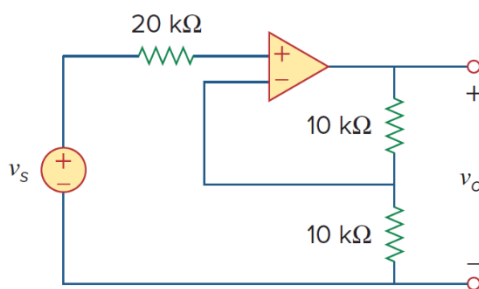2. The op amp in the following circuit is ideal. Find the closed loop gain ( $v_o/v_s$ ) of the following circuit.



**Answer:  $v_o/v_s = 2$**

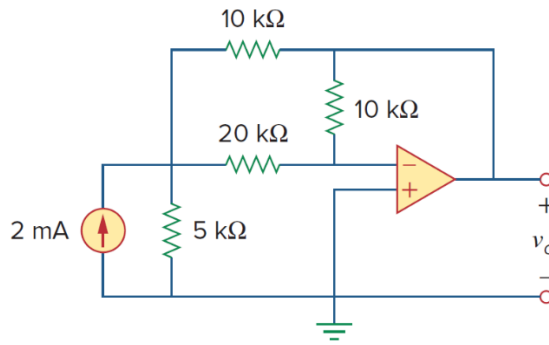
3. The op amp in the following circuit is ideal. Determine the output voltage  $v_o$  in the following circuit.



**Answer:  $v_o = -2.5 \text{ V}$**

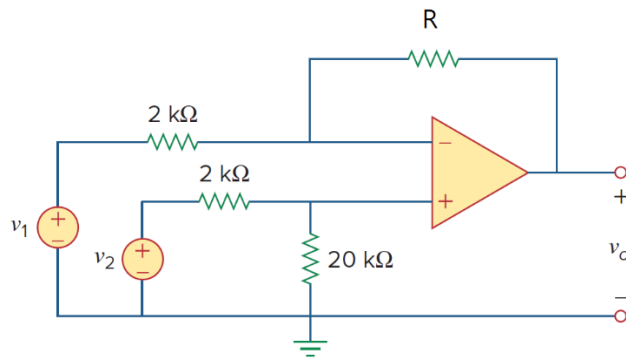4. The op amp in the difference amplifier circuit below is ideal.
- Find  $v_o$  and CMRR given that  $v_1 = 1 \text{ V}$ ,  $v_2 = 2 \text{ V}$ , and  $R = 20 \text{ k}\Omega$ .
  - Find  $v_o$  and CMRR given that  $v_1 = 1 \text{ V}$ ,  $v_2 = 2 \text{ V}$ , and  $R = 19 \text{ k}\Omega$ .
  - Which circuit in (a) and (b) is better? Why?

(Round the solutions to 2 decimal places)



**Answers (a)  $v_o = 10 \text{ V}$ ,  $\text{CMRR} = \infty$ . (b)  $v_o = 9.59 \text{ V}$ ,  $\text{CMRR} = 211.56$**